


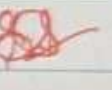





INDEX

S. No.	Date	Name of the Experiment	Page No.	Marks Awarded	Signature
1	06.11.24	Verification of Kirchhoff's law.	1-5	10	
2	20.11.24	OPEN CIRCUIT AND LOAD CHARACTERISTICS OF DC SHUNT GENERATOR.	7-17	10	
3	02.11.24	STAIRCASE WIRING	19-21	10	
4	11.12.24	HALF WAVE AND FULL WAVE RECTIFIER.	23-31	10	
5	18.12.24	ZENER DIODE VOLTAGE REGULATOR.	33-37	10	
6	23.12.24	CHARACTERISTICS OF LVDT	39-45	10	

CIRCUIT DIAGRAM: KCL:-

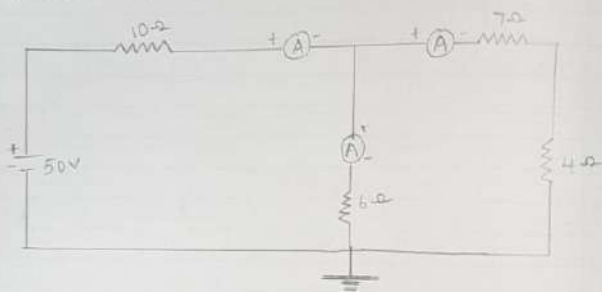

TABULATION:-

KCL	$I_a(A)$	$I_b(A)$	$I_c(A)$	$I_b + I_c (A)$
THEORETICAL	3.601	2.33	1.271	3.601
PRACTICAL	3.602	2.33	1.271	3.602

Expt. No. 1

Page No. 1

VERIFICATION OF KIRCHHOFF'S LAW

AIM:-

To verify Kirchhoff's Current law and Kirchhoff's Voltage law of circuit.

SOFTWARE REQUIRED:-


Multisim [12.0]

THEORY:-

KVL:- Kirchhoff's law states that the sum of the voltage differences around any closed loop in a circuit must be zero. A loop in a circuit is any path which ends at the end at the same point at which it starts.

KCL:- Kirchhoff's Current law states that the algebraic sum of the current entering and leaving a node is equal to zero. By convention, currents entering the node are positive and those leaving a node are negative.

CIRCUIT DIAGRAM:-

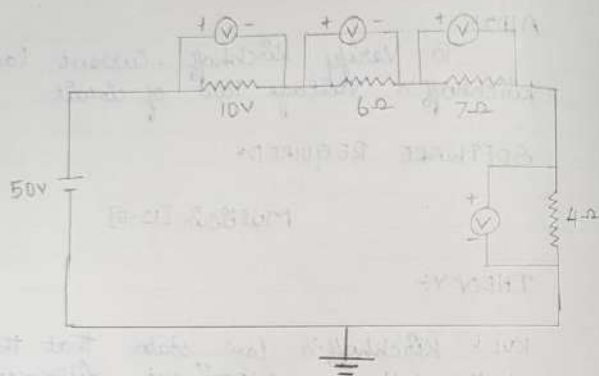

TABULATION:-

KVL	SOURCE (V)	$V_{10\Omega}$ (V)	$V_{6\Omega}$ (V)	$V_{7\Omega}$ (V)	$V_{4\Omega}$ (V)
THEORETICAL	50	36.01	13.98	0	0
PRACTICAL	50	38.51	11.11	7.407	12.968

Expt. No.

Page No. 3

KCL:-

To prove,

At Node A,

$$I_a = I_b + I_c$$

$$I_b = 2.33A$$

$$I_c = 1.271A$$

$$I_a = 3.601A$$

$$\therefore I_a = I_b + I_c$$

$$3.601A = 2.33A$$

KVL:-

LOOP 1:-

$$50 = V_{10\Omega} + V_{6\Omega}$$

$$V_{10\Omega} = I_{10\Omega} \times 10$$

$$V_{6\Omega} = 6(I_1 - I_2)$$

$$50 = 10I_1 + 6(I_1 - I_2)$$

$$50 = 16I_1 - 6I_2 \Rightarrow (1)$$

LOOP 2:-

$$0 = 4I_2 + 4I_2 + 6(I_2 - I_1)$$

$$= 14I_2 + 6(I_2 - I_1)$$

$$= 14I_2 - 6I_1 \Rightarrow (2)$$

$$\begin{bmatrix} 16 & -6 \\ -6 & 14 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 50 \\ 0 \end{bmatrix}$$

$$I_1 = 3.6014 \text{ A}$$

$$I_2 = 1.2714 \text{ A}$$

$$V_{10-2} = I_{10-2} \times 10 = 3.6014 \times 10 = 36.01 \text{ V}$$

$$\begin{aligned} V_{6-2} &= I_{6-2} \times 6 = (I_1 - I_2) \times 6 \\ &= (3.601 - 1.271) \times 6 \\ V_{6-2} &= 13.98 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{To prove: } 50 &= V_{10-2} + V_{6-2} \\ &= 36.01 + 13.98 \\ &= 49.99 \text{ V} \end{aligned}$$

10

8

RESULT:-

Thus, The Kirchhoff's Current law and Kirchhoff's Voltage law were verified successfully.

$$\begin{aligned}
 A_{\text{shunt}} &= I \\
 A_{\text{arm}} &= I \\
 V_{\text{oc}} &= E - I_a R_a - I_f R_f = E - I_a R_a \\
 E &= V + I_a R_a + I_f R_f \\
 V &= E - I_a R_a - I_f R_f \\
 V &= E - I_a R_a - I_f R_f
 \end{aligned}$$

not found any other info about this experiment

Expt. No. 2

Page No. 7

OPEN CIRCUIT AND LOAD CHARACTERISTICS OF DC SHUNT GENERATOR.

AIM:-

To draw the open circuit and load characteristics of DC Shunt generator.

APPARATUS REQUIRED:-

Laptop with internet connection.

THEORY:-

DC generator converts mechanical energy into electrical energy.


DC generator works on the principle of Faraday's law. It states that "When a conductor cuts the magnetic flux and EMF is induced."

The field winding and armature winding are connected in parallel in the shunt generator.

OPEN CIRCUIT CHARACTERISTICS:-

It is also known as magnetisation characteristics or no load characteristics. It is a graph drawn between open circuit voltage (E_o) and field current (I_f).

OPEN CIRCUIT CHARACTERISTICS:-

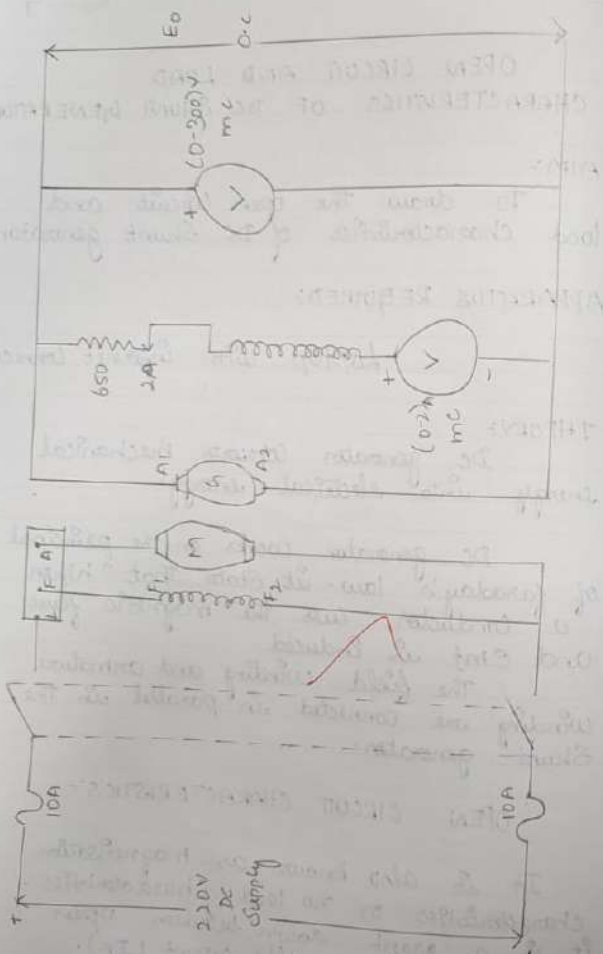

Expt. No.

Page No. 9

LOAD CIRCUIT CHARACTERISTICS:-


It is a graph drawn between load voltage (V_L) and load current (I_L). It is also known as external characteristics.

OPEN CIRCUIT CHARACTERISTICS:-

1. Connections are made as per the circuit diagram.
2. Switch on the supply and note down the reading (voltage and current).
3. By varying the field rheostat different values of open circuit voltage are noted.
4. Plot the graph b/w open circuit voltage and field current.

MODEL GRAPH

OPEN CIRCUIT CHARACTERISTICS:-

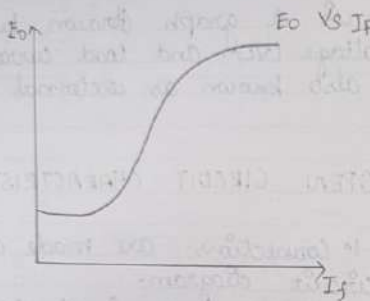

S.No	VOLTAGE	CURRENT (A)
1	115	0.16
2	120	0.18
3	126	0.20
4	129	0.21
5	133	0.23
6	135	0.24
7	138	0.27
8	142	0.30


11

Open circuit characteristics


Scale

X-axis: 1 cm = 0.02 A

Y-axis: 1 cm = 10 V

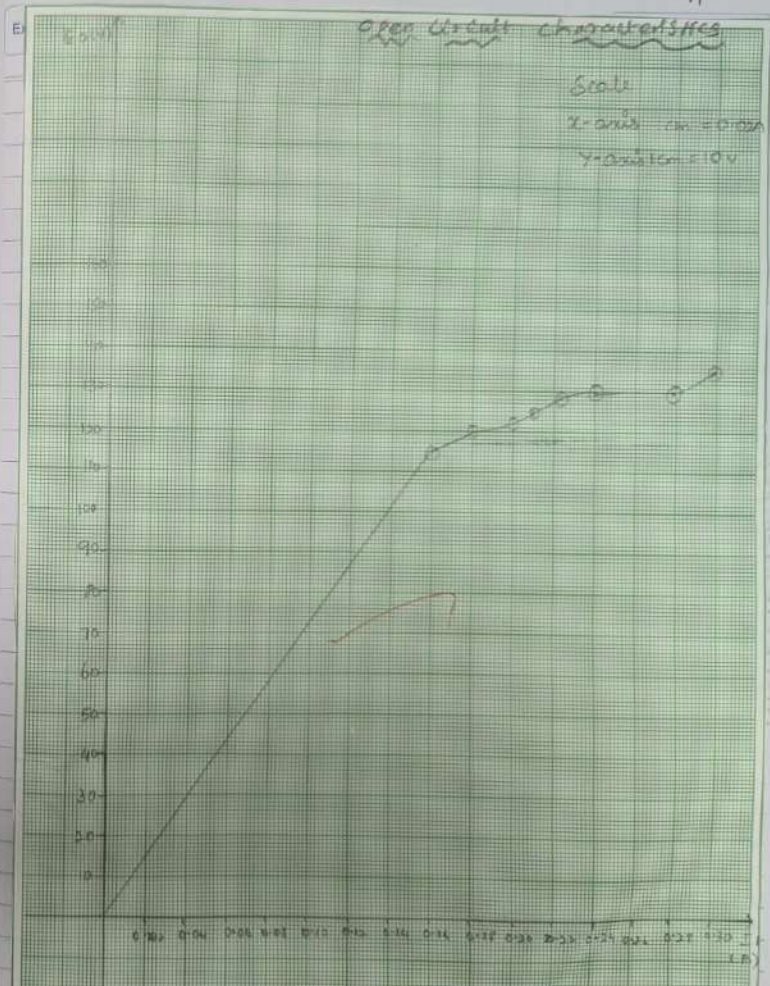

LOAD CIRCUIT CHARACTERISTICS:-

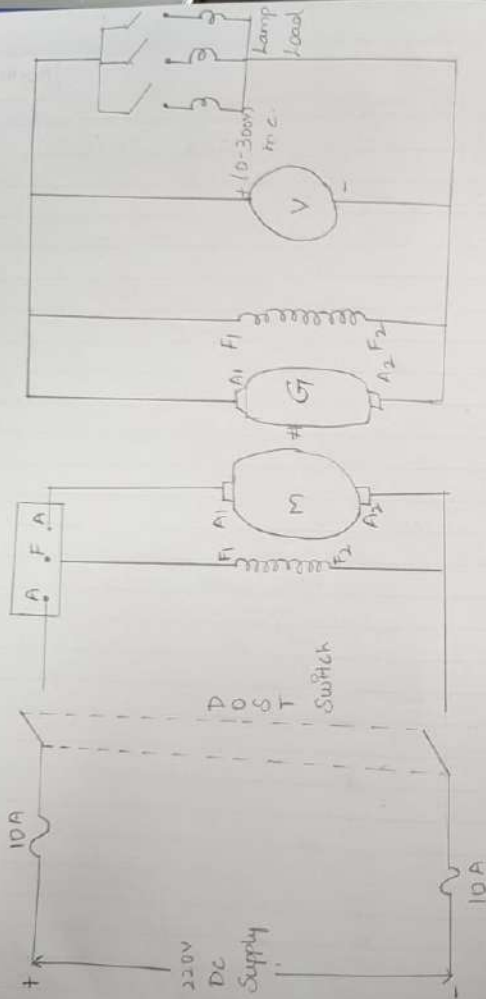

Expt. No.


Page No. 13

LOAD CHARACTERISTICS:-

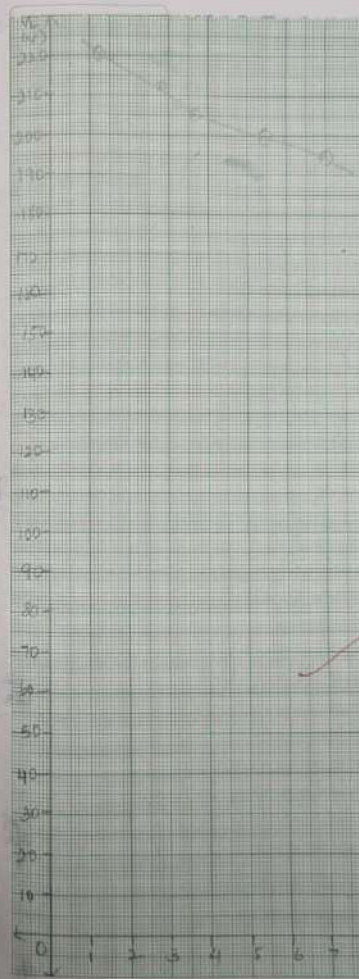1. Connections are made as per the circuit diagram.
2. Switch on the supply and note the no load voltage and current.
3. By connection different nodes, different values of load voltage and current are noted.
4. plot the graph between load voltage and load current.

Load Characteristics

Scale:
x-axis: 1cm = 1A
y-axis: 1cm = 10V




LOAD CHARACTERISTICS

1. Plot the graph between load voltage and load current.
2. By measuring different values of load voltage and load current, draw the graph.
3. Plot the graph between load voltage and load current.

MODEL GRAPH

Load Characteristics

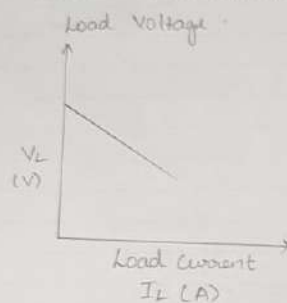

S.No	Current (A)	Voltage (V)
1	1.2	220
2	2.8	212
3	3.2	208
4	3.6	205
5	5.5	200
6	7	195


Expt. No.

Page No. 17

RESULT :-

Thus the open circuit and load characteristics of DC shunt generator were verified successfully.

CIRCUIT DIAGRAM:-

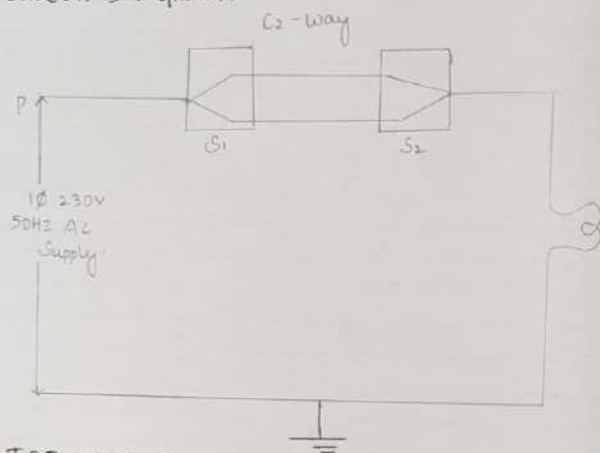

TABULATION:-

Mode	S ₁	S ₂	Lamp
1	OFF	OFF	ON
2	OFF	ON	OFF
3	ON	OFF	OFF
4	ON	ON	ON

Expt. No. 3

Page No. 19

STAIRCASE WIRING

AIM:-

Draw the staircase wiring diagram and develop it in proteus.

APPARATUS REQUIRED:-

Laptop with proteus.

THEORY:-


Staircase wiring is a common multiple way switching or two way switching connection. It involves wiring for one light with two switches. In this setup a single lamp is controlled by two switches located at different position. It allows the user to operate the load from separate position above or below the staircase from inside or outside of room or two way bed switch.

PROCEDURE:-

1) Drag the required components from the proteus library.

2) Connect the components as per circuit diagram.

CROSS CONNECTION:

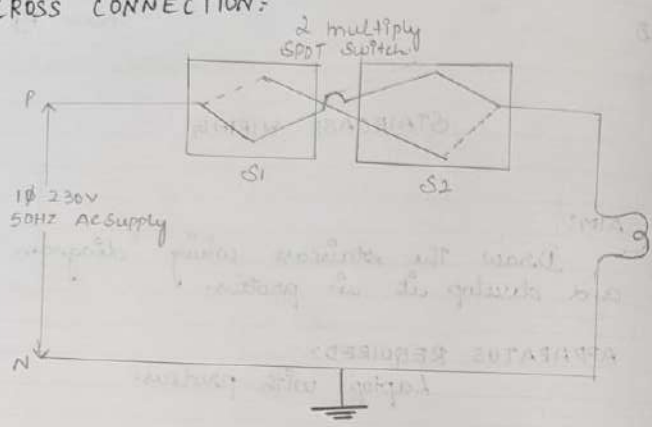

TABULATION:

Mode	S ₁	S ₂	Lamp
1	OFF	OFF	OFF
2	OFF	ON	ON
3	ON	OFF	ON
4	ON	ON	OFF

Components	Proteus	Specification
AC Supply	V _{sine}	Amplitude = 230V Frequency = 50Hz
2 way S/W	SPDT	
LAMP	Lamp (Animated)	230V

Expt. No.

Page No. 2-1

3) Run the Simulation and check the lamp for different switch condition.

10


RESULT:

Thus the staircase wiring connection are developed in proteus and tested.


HALF WAVE RECTIFIER:-

Circuit Diagram:-

Without filter:-

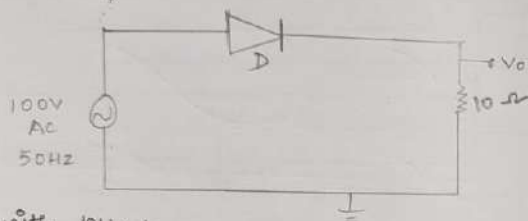

With filter:-

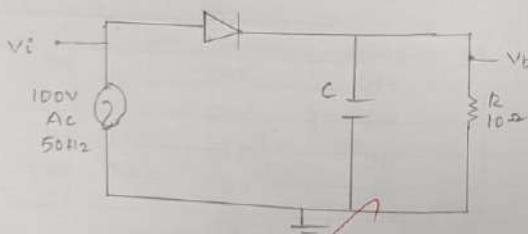

Input Voltage		Output Voltage			
		Without filter		With filter	
$V_m(V)$	$t(ms)$	$V_m(V)$	$t(ms)$	$V_m(V)$	$t(ms)$
100V	20ms	100V	10ms	100V, 85V	5ms, 15ms

Expt. No. 4

Page No. 23

HALF WAVE AND FULL WAVE

AIM:-

To simulate the following circuits
 (i) Half wave rectifier
 (ii) Full wave rectifier

APPARATUS REQUIRED:-

Laptop with Proteus Software



THEORY:-

A rectifier is a circuit that converts alternating current (AC) into Direct current (DC).

HALF Wave rectifier:-


Half wave rectifier conducts only during positive half cycle. During positive half cycle, the diode current and the output voltage is equal to the voltage. During negative half cycle, the diode does not conduct and the output voltage is equal to zero.

MODEL GRAPH:-

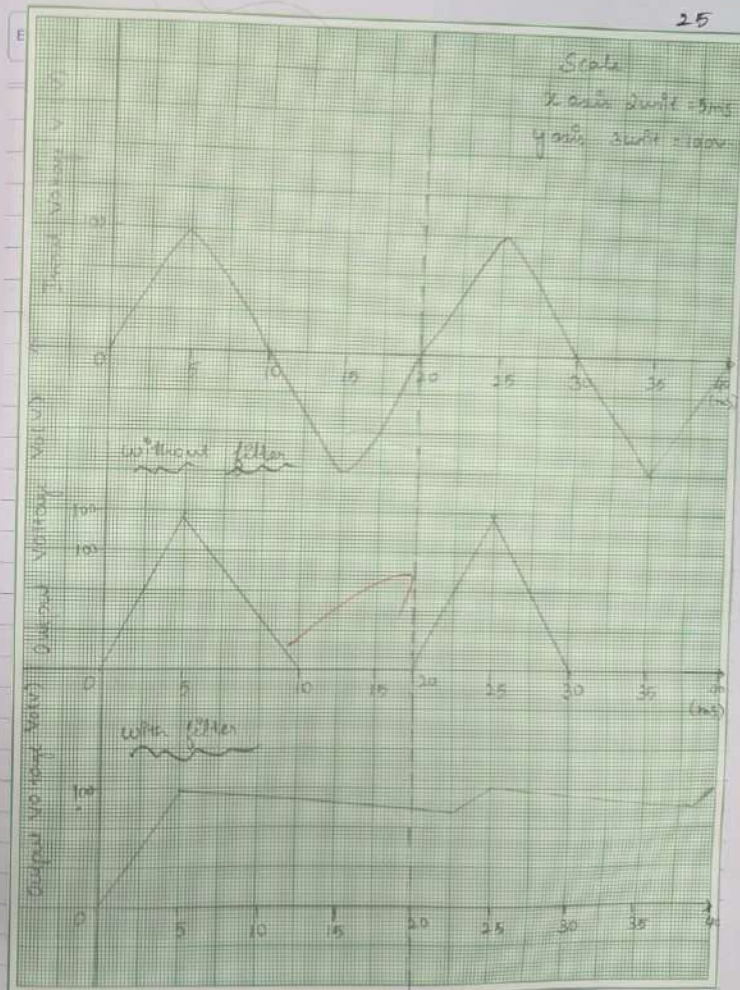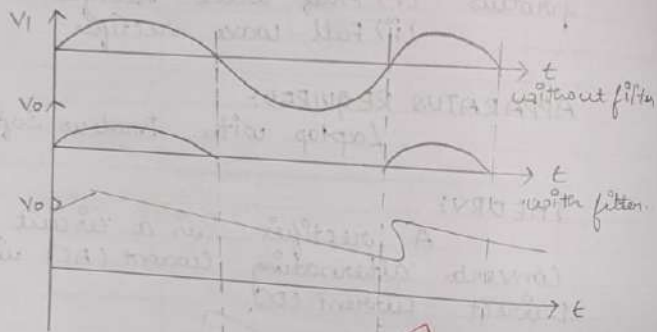


FULL WAVE RECTIFIER:

Circuit diagram:
without filter

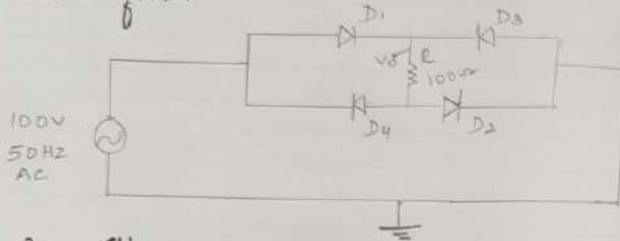

with filter

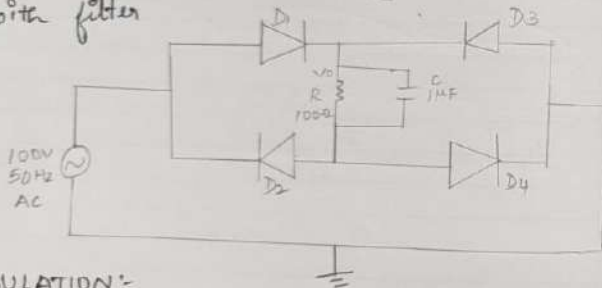

TABULATION:-

Input Voltage		Output Voltage			
		without filter.		with filter	
V_m (V)	t (ms)	V (V)	t (ms)	V_m (V)	t (ms)
50V	20ms	50V	5ms	50V, 46V	5ms, 14ms

Expt. No.

Page No. 27

FULL wave rectifier:



Full wave rectifier conducts during both +ve and -ve half cycles. During +ve half cycle, the output voltage is equal to input voltage. During negative half cycle, the output voltage is equal to negative of the input voltage.

The output of the rectifier circuit is impure DC. In order to get, pure DC the output is filtered by a capacitor filter.

PROCEDURE:-

- 1) Drag the required components from the proteus library.
- 2) Connect the components as per the circuit.
- 3) Measure the input and output voltage and note in tabulation.

MODEL GRAPH:-

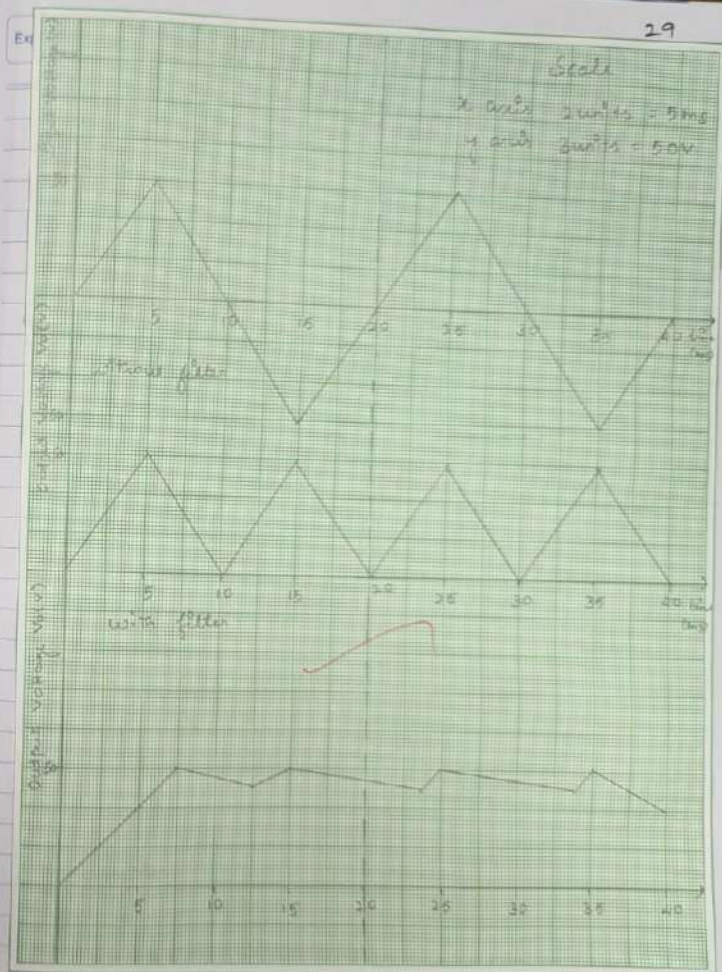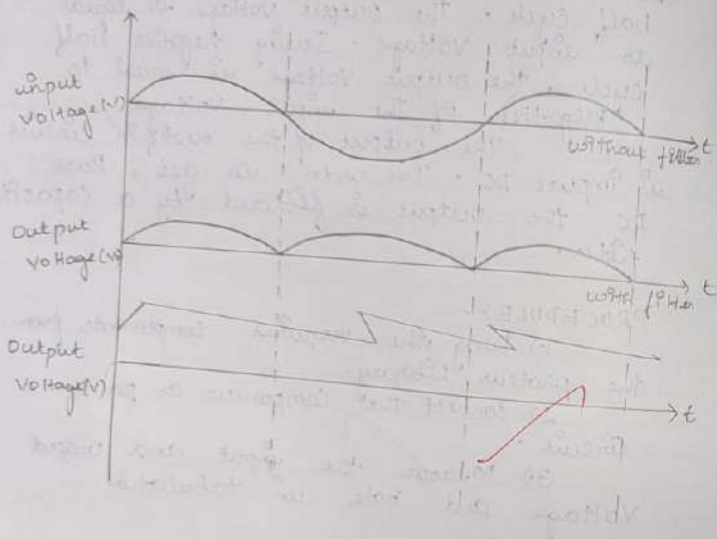

COMPONENTS REQUIRED:-


S.No	Components	Proteus VSource	Specification
1.	AC Supply		Amplitude = 10V Frequency = 50Hz
2.	Diode	Generic diode	
3.	Resistor	Analog resistor primitive	100Ω
4.	Capacitor	Generic Non-electrolytic Capacitor	1 microF
5.	Ground	From terminal node	
6.	Probe	From Probe made Voltage.	
7.	Graph	From Graph made Analogue.	

RESULT:-

Stimulation of both half-wave and full-wave rectifiers was successful.

LINE REGULATION:-


CIRCUIT DIAGRAM:-

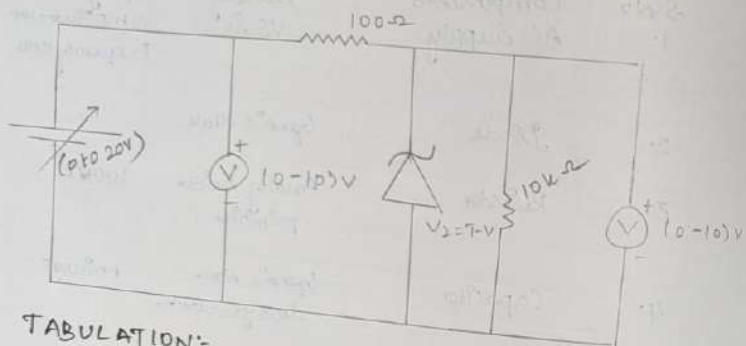

TABULATION:-

S. No	Input Voltage V_i (V)	Output Voltage V_o (V)
1	+12.0	+5.4
2	+13.0	+5.16
3	+14.0	+5.17
4	+15.0	+5.17
5	+16.0	+5.18
6	+17.0	+5.19

MODEL GRAPH:-

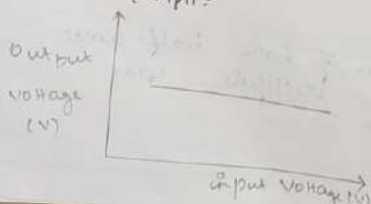

Expt. No. 5

Page No. 33

ZENER DIODE AS VOLTAGE REGULATOR.

AIM:-

To simulate that line and load regulation operation zener diode.

APPARATUS REQUIRED:-

Laptop with proteus software.

THEORY:-


A Heavily doped PN Junction diode is called Zener diode. Due to heavily doped nature Zener diode works under forward bias and reverse bias conditions.

Zener diode under reverse bias condition is used as a voltage regulator. If the input voltage changes the output is constant. This is called line regulation.

The load resistance changes the output voltage is constant this is called load regulation.

LOAD REGULATION:-


CIRCUIT DIAGRAM:-

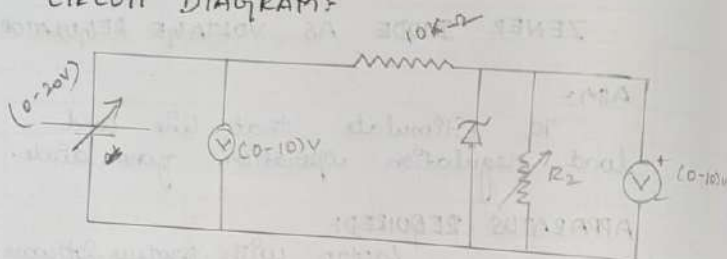

TABULATION:-

S.NO	Load Resistance $R_2(\Omega)$	Output Voltage $V_o(V)$
1	+17.0 (100 Ω)	+5.19
2	+17.0 (200 Ω)	+5.20
3	+17.0 (300 Ω)	+5.20
4	+17.0 (400 Ω)	+5.20
5	+17.0 (500 Ω)	+5.20
6	+17.0 (600 Ω)	+5.21

MODEL GRAPH:-

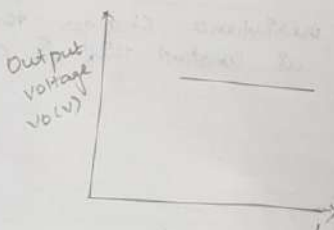

Expt. No.

Page No. 35

PROCEDURE:-

- 1) Drag the required components from the proteus library.
- 2) Connect the components (required) as per circuit diagram.
- 3) For line regulation vary the input voltage and note the output voltages in tabulations. Draw the graph between input and output voltages.
- 4) For load regulation vary the load resistance and note the output voltage in tabulation. Draw the graph between load resistance and voltage.


10

~~10~~

RESULT:-

Thus stimulation of line regulation operation of clonal dioside successfully completed.

Circuit Diagram:-

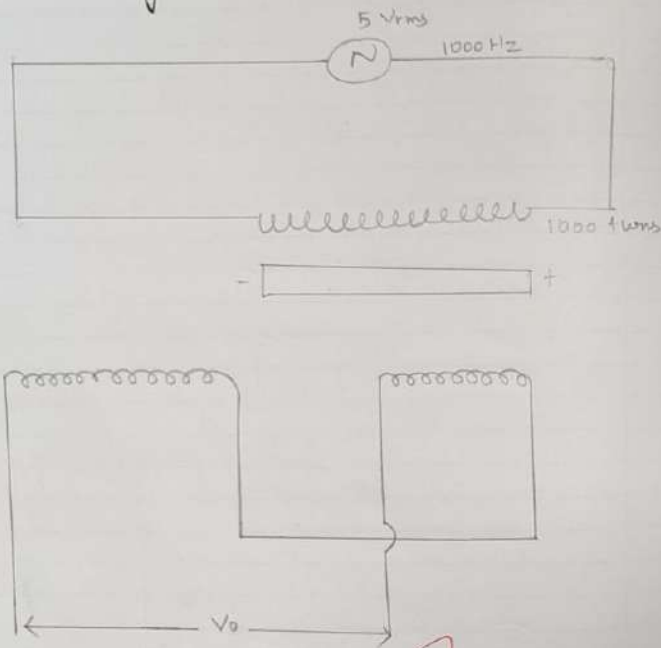

TABULATION:-

	Input Voltage (mV)	Output Voltage (V)	Frequency (Hz)	Time = $1/f$ (ms)
Positive displacement.	7	2.2	1000	1
Negative displacement.	7	2.2	1000	1

Expt. No. 6

Page No. 39

CHARACTERISTIC OF LVDT [LINEAR VARIABLE DIFFERENTIAL TRANSFORMER]

AIM:-

TO understand and simulate the reaction between core displacement and output voltage.

APPARATUS REQUIRED:-

Laptop with Internet Connection.

THEORY:-

LVDT is an inductive transducer that converts linear displacement into a electrical signal. It consist of a transformer having primary winding and two secondary windings wound on a core. As the primary is connected to an AC source. The AC current and the voltage are produced in the Secondary of the LVDT.

When the core is at the center, the flux linking with both the secondary winding are equal. So, the EMF induced in both the windings are equal this mean there is no displacement.

CALCULATION:-

$$V_m = V_{rms} \times \sqrt{2} = 5\sqrt{2} = 7V$$

$$4SD = 7V$$

$$1SD = 7/4 V$$


$$1.2SD = 7/4 \times 1.25 = 2.2V$$

$$f = 1000 \text{ Hz}$$


$$T = 1/f = 1/1000 = 1 \text{ ms}$$

MODEL GRAPH:-

Positive displacement:-

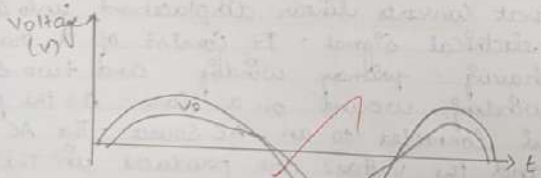

Negative displacement:-

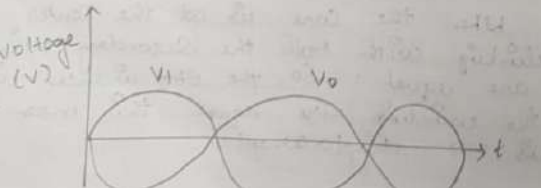

Expt. No.

Page No. 41

When the core is at the right, the flux linkage with the secondary winding S_1 is more so, the emf induced in S_1 is more than S_2 . So the emf is positive.

When the core is at the left, the flux linkage and the emf in S_2 is more than S_1 . So the net emf is negative.

PROCEDURE:-

1) Connections are made as per the circuit diagram.

2) Set the number of turns, Supplied voltage.

3) Configure the parameters.

4) Move the core to positive side and the negative side and observe the input voltage and output voltage waveforms.

5) plot the graph between input and output voltage.

43

On 7-0-00 500 mg
On 7-0-00 1000 mg



2. $\frac{1}{2}$ Kreis $\frac{1}{2} \cdot 2\pi = \pi$ cm

$$\text{Sn} + \text{V} \rightarrow \text{Sn}^{2+} + \text{V}^{3+}$$


Expt. No.

Page No.

45

10



RESULT:-

The relation between core displacement and output voltage is simulated successfully.